

EE 236 Devices Lab

Lab - 04

Anupam Rawat, 22b3982

31st August, 2024

I/V Characteristics of a Solar Cell

1 Measurement of I-V Characteristics

1.1 Aim of the experiment

Measure the I-V Characteristics of the Solar Cell under different Illumination conditions.

1.2 Design

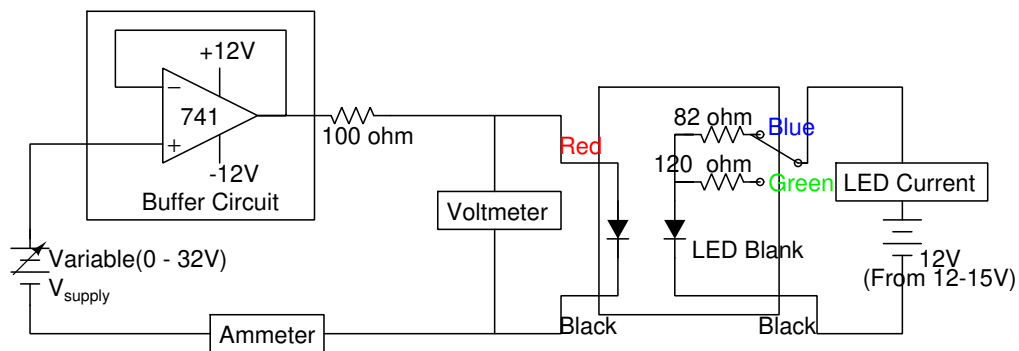


Figure 1: Caption

1.3 Dark I-V Conditions

Vd	Id	Vd	Id	Vd	Id
0.0073	0.1	0.295	1	0.348	2
0.234	0.4	0.312	1.2	0.355	2.3
0.255	0.5	0.329	1.5	0.358	2.5
0.28	0.8	0.333	1.6	0.366	2.8
0.341	1.8				

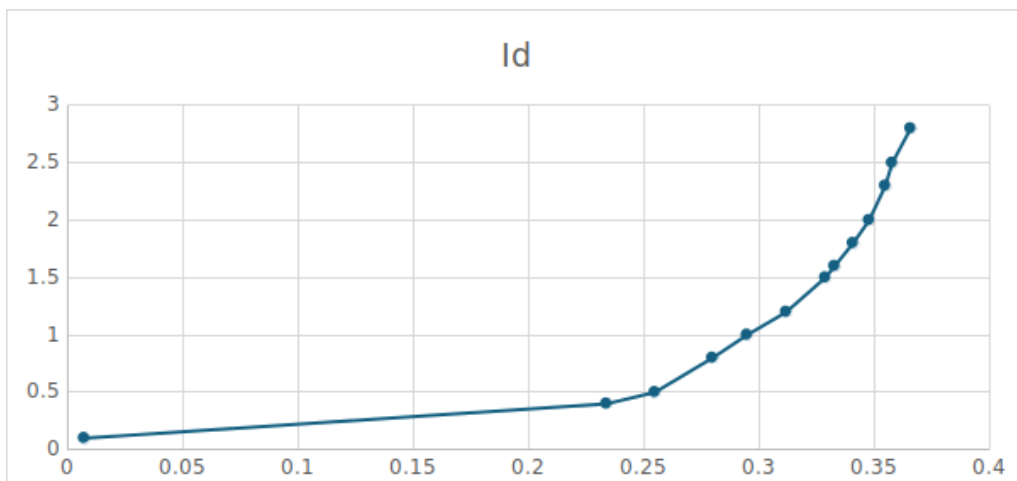


Figure 2: Dark I/V Characteristic

1.4 Green I-V Solar Cell Characteristics

V_d	I_d	V_d	I_d	V_d	I_d
0.426	0.1	0.448	3	0.465	6
0.43	0.8	0.453	3.9	0.468	6.5
0.436	1.4	0.46	4.7	0.469	6.8
0.445	2.6	0.463	5.4	0.471	7.3

Table 1: I-V characteristics data of Green LED

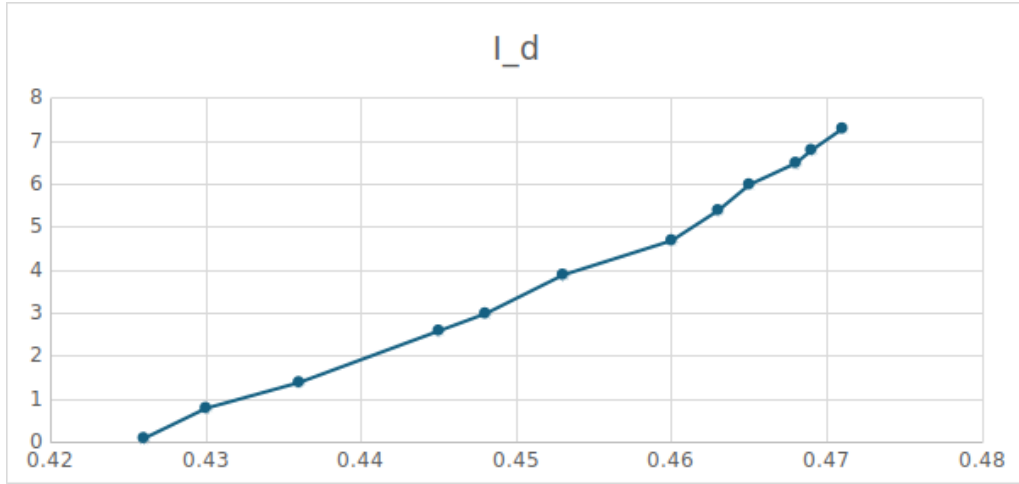


Figure 3: Green I/V Characteristic

1.5 Blue I-V Solar Cell Characteristics

V_d	I_d	V_d	I_d	V_d	I_d
0	0	0.35	2.7	0.41	6.2
0.09	0.1	0.38	3.9	0.42	6.9
0.3	1	0.39	4.7	0.434	7.6
0.33	1.7	0.4	5.5		

Table 2: I-V characteristics data of Blue LED

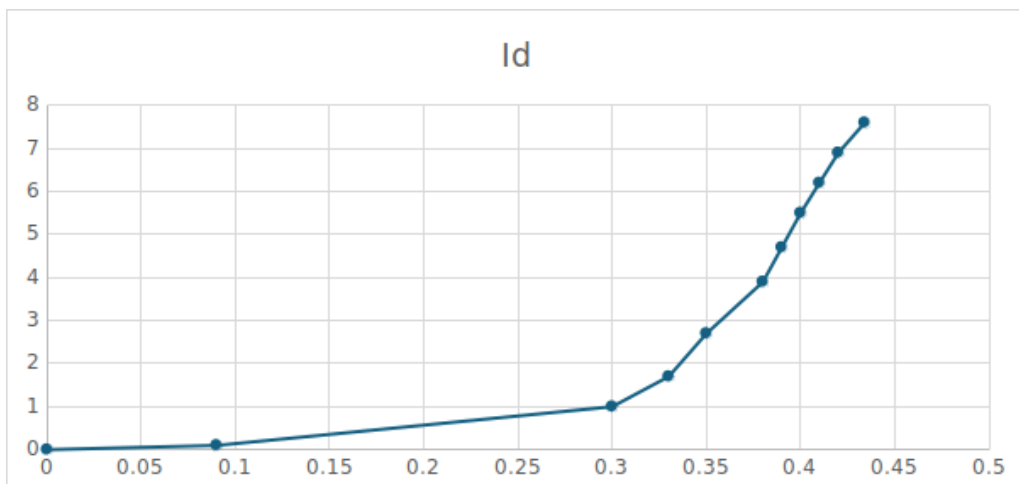


Figure 4: Blue I/V Characteristic

2 Solar cell as power source

2.1 Aim of the Experiment

Investigate the use case of Solar Cell as a power source for different intensities namely I_1 for Green and I_2 for Blue.

2.2 Design

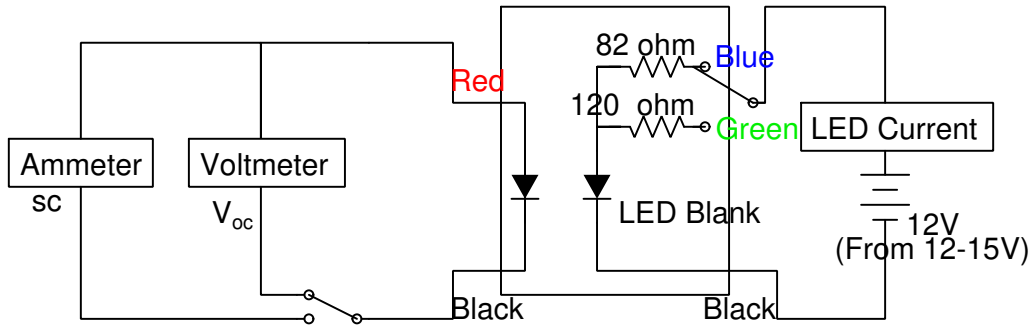


Figure 5: Caption

2.3 Simulation

2.3.1 Code

Solar Cell description was given in a file format

```
.include "./solar_cell.txt"
```

```
Vs 0 1 dc 0
```

```
r1 2 0 100
```

```
x1 1 2 solar_cell
```

```
.dc Vs -2 2 0.01
```

```
.control
```

```
run
```

```
plot V(2)/100 vs V(1) - V(2), (V(1) - V(2))*V(2)/100 vs V(1) - V(2)
```

```
.endc
```

```
.end
```

2.3.2 Results

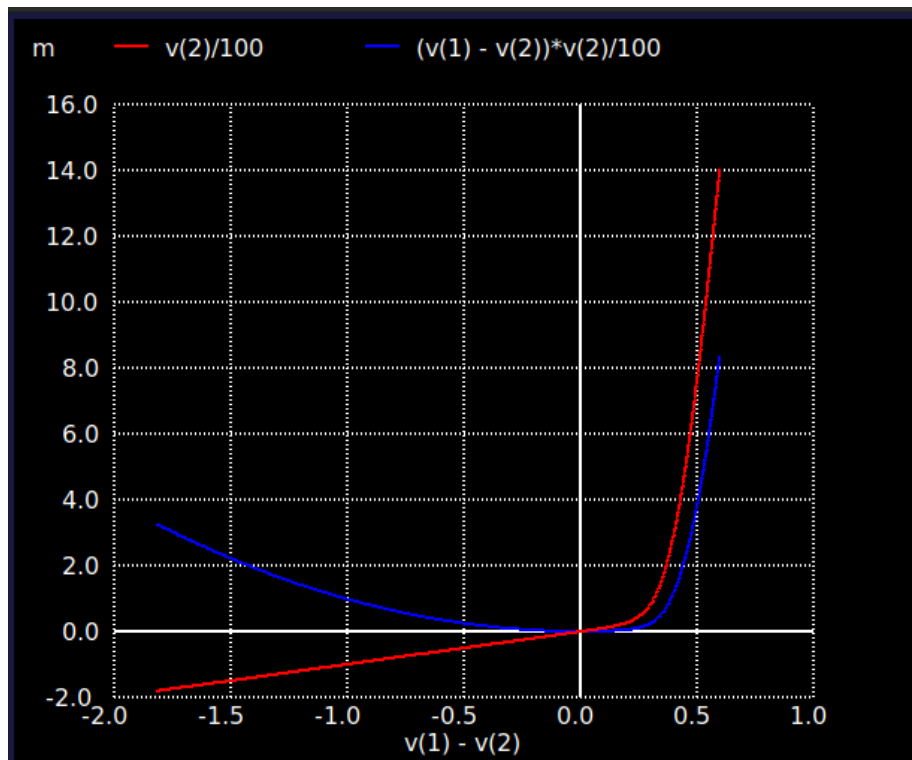


Figure 6: Simulation Results of Dark I-V Characteristics

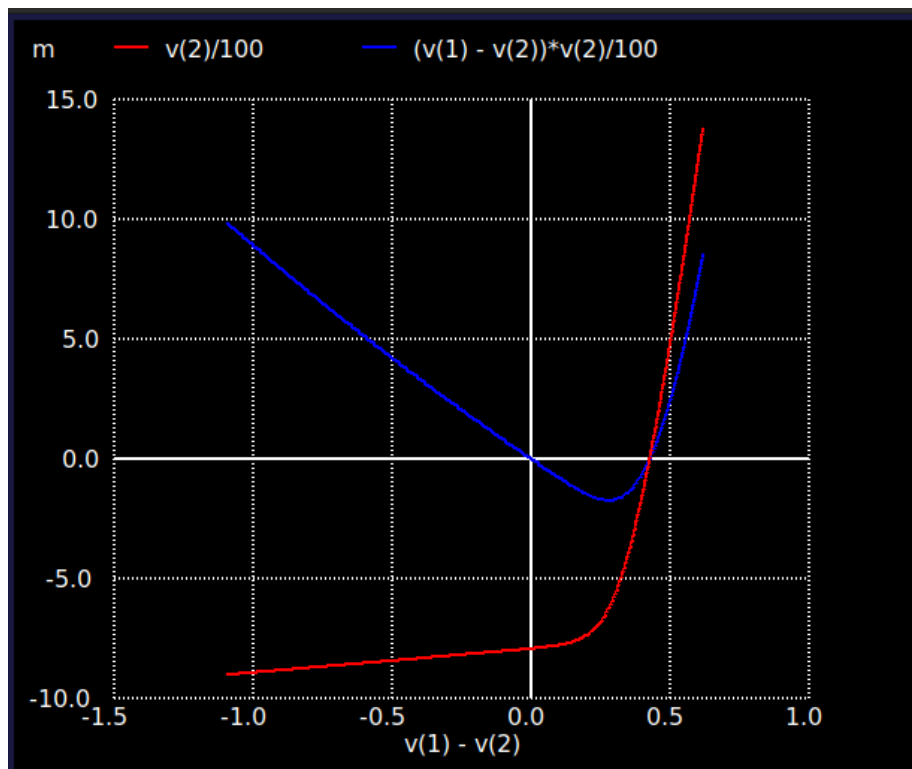


Figure 7: Simulation Results of Illumination 1 (Green) I-V Characteristics

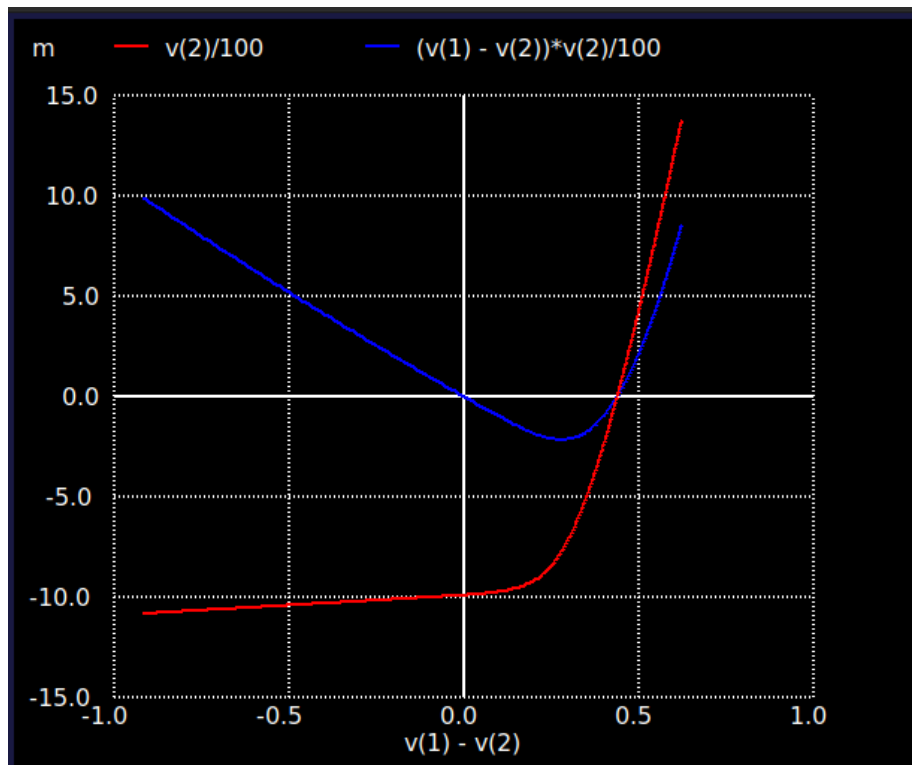


Figure 8: Simulation Results of Illumination 2 (Blue) I-V Characteristics

2.4 Experimental Results

V_L	I_L	V_L	I_L	V_L	I_L
0.084	6.43	0.282	5.85	0.346	4.83
0.152	6.38	0.307	5.59	0.382	3.62
0.228	6.2	0.323	5.32	0.395	3.03
0.255	6.07	0.336	5.02	0.402	2.61
0.407	2.13	0.412	1.93	0.45	1
0.46	0.05				

Table 3: Using Solar Cell as a power source for Intensity I_1 Green

V_L	I_L	V_L	I_L	V_L	I_L	V_L	I_L
0.131	10.33	0.314	9.29	0.402	6.2	0.442	2.54
0.212	10.15	0.334	8.91	0.611	5.62	0.447	1.92
0.259	9.9	0.362	8.16	0.421	4.84	0.434	3.56
0.289	9.65	0.377	7.5	0.429	4.03	0.447	1.8
0.297	9.52	0.391	6.82	0.439	2.94		

Table 4: Using Solar Cell as a power source for Intensity I_2 Blue

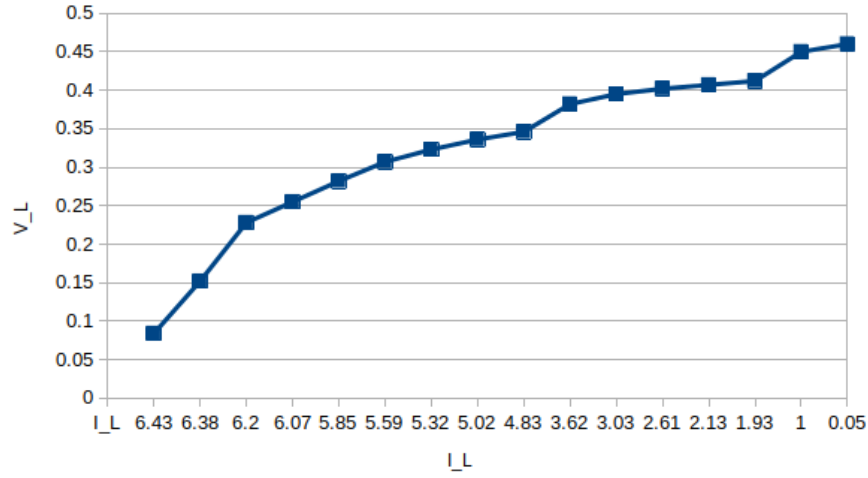


Figure 9: Experimental Results of Illumination 1 (Green) I-V Characteristics

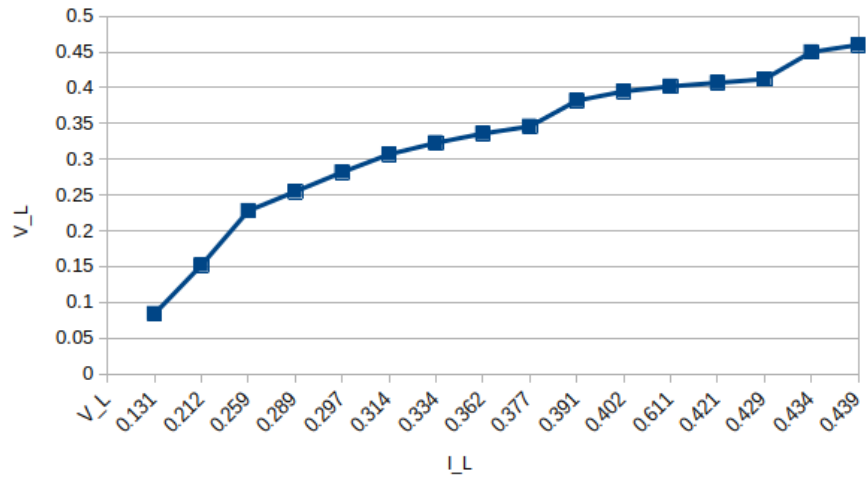


Figure 10: Experimental Results of Illumination 1 (Blue) I-V Characteristics

2.5 Equations and Formulas

The Fill Factor for a Solar Cell is given by the ratio of maximum power to the product of Short Circuit Current (I_{sc}) and Open Circuit Voltage (V_{oc})

$$FF = \frac{I_{MP} \times V_{MP}}{I_{sc} \times V_{oc}} \quad (1)$$

2.6 Results

	(Sim) I_{sc}	(Sim) V_{oc}	(Sim) P_{max}	(Exp) I_{sc}	(Exp) V_{oc}	(Exp) P_{max}	(Sim) FF	(Exp) FF
Green	-0.003571 mA	1 V	0.47619 μ W	6.43 mA	0.46 V	1.71836 mW	0.133	0.581
Blue	-0.003839 mA	0.440678 V	0.44643 μ W	10.33 mA	0.447 V	3.43382 mW	0.264	0.744

Table 5: Comparison of Simulated and Experimental Data for Different Illumination Intensities

3 Measurement of V_{OC} and I_{SC} at different illumination levels

3.1 Circuit Design

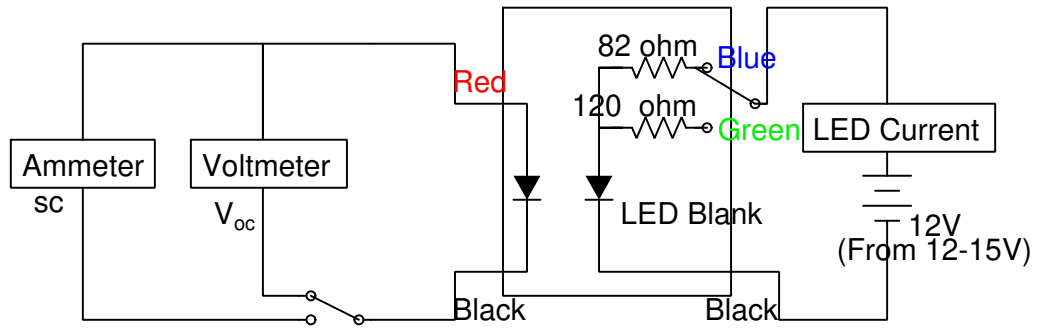


Figure 11: Experiment 3

3.2 Experimental Results

Vsupply (V)	I _{led} (mA)	V _{oc} (V)	I _{sc} (mA)
6.28	10	0.36	1.84
7.49	20	0.41	3.78
8.67	30	0.43	5.74
9.83	40	0.44	8.01
10.98	50	0.46	9.88

Table 6: Vsupply, I_{led}, V_{oc}, and I_{sc} measurements